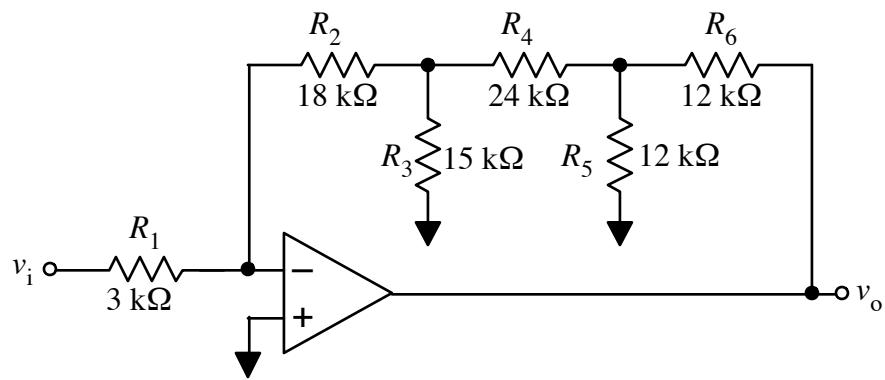


For the circuit shown below, calculate the value of the gain,  $G = v_o/v_i$ . The op amp is ideal.



$$G = \underline{\hspace{2cm}}$$

(a number)