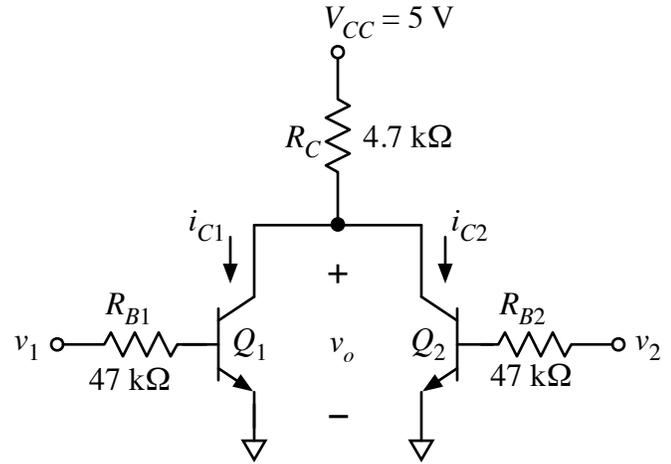
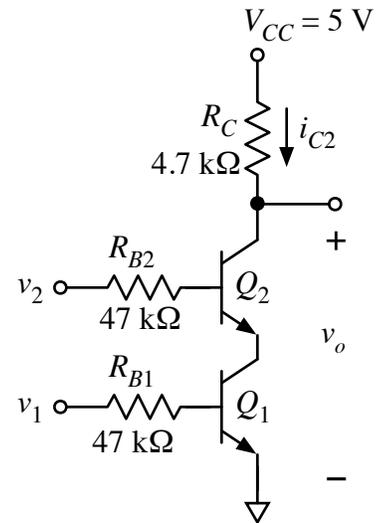


- a. For the circuit at right, the input voltages,  $v_1$  and  $v_2$ , can be either 0 V or 5 V. Calculate  $v_o$  for all four possible combinations of  $v_1$  and  $v_2$ . The two BJTs are identical with  $\beta_F = 100$ . (Don't panic. Make a reasonable guess for BJT modes — off, FA, or sat — and check. Patterns will quickly become evident.)



$v_1$	0 V	5 V	0 V	5 V
$v_2$	0 V	0 V	5 V	5 V
$v_o$				

- b. For the circuit at right, the input voltages,  $v_1$  and  $v_2$ , can be either 0 V or 5 V. Calculate  $v_o$  for all four possible combinations of  $v_1$  and  $v_2$ . Same BJTs as part a.



$v_1$	0 V	5 V	0 V	5 V
$v_2$	0 V	0 V	5 V	5 V
$v_o$				

Put your answers — and whatever work will fit — on this sheet. Staple any sheets with additional work behind.